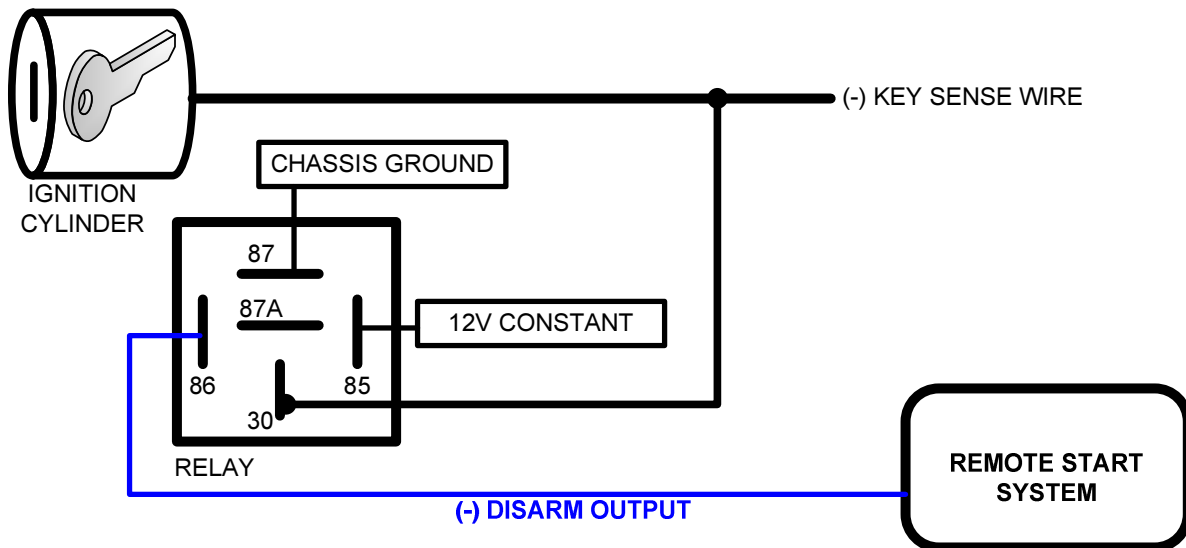


## FACTORY ALARM DISARM (KEY-SENSE WIRE)



Pictured left is the location of the key sense wire in a small connector by the ignition key cylinder on a 2001 Toyota 4Runner. On most vehicles, the key sense wire can be found in a small connector near the vehicle's ignition cylinder

- ▶ To disarm the factory security by connecting to the (-) key sense wire, use a relay and wire as shown:



PIN	CONNECTION
85	TO 12V CONSTANT
86	TO (-) FACTORY DISARM OUTPUT FROM SYSTEM
87	TO CHASSIS GROUND
87A	NO CONNECTION
30	TO KEY SENSE WIRE

Remote starter and security installations should be attempted by experienced security installers only. Information contained is accurate to the best of our knowledge and experience. Information contained is without any representation of warranty. It is the installer's responsibility to test and confirm all circuits with a digital multi-meter. Proper installation remains the responsibility of the installer. CarInstallExperts.com assumes no liability or responsibility resulting from an improper installation, even in reliance with the information contained in this guide.